

Finite State Machine Design #0

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **000000**

Input for testing: **10010000000110000001**

Finite State Machine Design #2

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **000010**

Input for testing: **1000001000010110000101**

Finite State Machine Design #4

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **000100**

Input for testing: **100001000100110001001**

Finite State Machine Design #6

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **000110**

Input for testing: **1000100011000110110001101**

Finite State Machine Design #8

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **001000**

Input for testing: **10010010001000010010001**

Finite State Machine Design #9

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **001001**

Input for testing: **10010001001001110010010**

Finite State Machine Design #10

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **001010**

Input for testing: **100100101001010110010101**

Finite State Machine Design #12

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **001100**

Input for testing: **10010011001100010011001**

Finite State Machine Design #14

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **001110**

Input for testing: **1001100111001110110011101**

Finite State Machine Design #16

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **010000**

Input for testing: **1010001000010000010100001**

Finite State Machine Design #17

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **010001**

Input for testing: **1010000100010001110100010**

Finite State Machine Design #18

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **010010**

Input for testing: **10100010010010110100101**

Finite State Machine Design #20

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **010100**

Input for testing: **10101010010100010101001**

Finite State Machine Design #21

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **010101**

Input for testing: **10101001010101110101010**

Finite State Machine Design #22

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **010110**

Input for testing: **10101011010110010101101**

Finite State Machine Design #24

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **011000**

Input for testing: **1011001100011000010110001**

Finite State Machine Design #25

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **011001**

Input for testing: **1011000110011001010110010**

Finite State Machine Design #26

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **011010**

Input for testing: **101101101011010010110101**

Finite State Machine Design #27

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **011011**

Input for testing: **101101011011011110110110**

Finite State Machine Design #28

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **011100**

Input for testing: **1011101110011100010111001**

Finite State Machine Design #29

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **011101**

Input for testing: **1011100111011101010111010**

Finite State Machine Design #30

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **011110**

Input for testing: **1011101111011110010111101**

Finite State Machine Design #33

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **100001**

Input for testing: **0100010000100001101000010**

Finite State Machine Design #34

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **100010**

Input for testing: **0100011000100010101000101**

Finite State Machine Design #35

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **100011**

Input for testing: **01000100011000111101000110**

Finite State Machine Design #36

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **100100**

Input for testing: **010010100100100001001001**

Finite State Machine Design #37

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **100101**

Input for testing: **010010010100101101001010**

Finite State Machine Design #38

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **100110**

Input for testing: **0100111001100110101001101**

Finite State Machine Design #39

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **100111**

Input for testing: **0100110011100111101001110**

Finite State Machine Design #41

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **101001**

Input for testing: **01010100101001101010010**

Finite State Machine Design #42

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **101010**

Input for testing: **01010110101010001010101**

Finite State Machine Design #43

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **101011**

Input for testing: **01010101101011101010110**

Finite State Machine Design #45

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **101101**

Input for testing: **01011101101101001011010**

Finite State Machine Design #46

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **101110**

Input for testing: **0101111011101110001011101**

Finite State Machine Design #47

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **101111**

Input for testing: **0101110111101111101011110**

Finite State Machine Design #49

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **110001**

Input for testing: **0110011000110001001100010**

Finite State Machine Design #51

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **110011**

Input for testing: **01101100110011101100110**

Finite State Machine Design #53

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **110101**

Input for testing: **011011010110101001101010**

Finite State Machine Design #54

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **110110**

Input for testing: **01101110110110001101101**

Finite State Machine Design #55

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **110111**

Input for testing: **01101101110111101101110**

Finite State Machine Design #57

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **111001**

Input for testing: **0111011100111001001110010**

Finite State Machine Design #59

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **111011**

Input for testing: **011110111011001110110**

Finite State Machine Design #61

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **111101**

Input for testing: **0111110111101001111010**

Finite State Machine Design #63

Develop a finite state machine (FSM) diagram to detect the particular binary pattern shown below. The input to your FSM is a sequence of binary bits that come in series at each clock cycle. When the FSM recognizes the bit pattern, the output is set to '1', otherwise it stays at '0'. Your FSM should be able to detect overlapped patterns. Use the following input sequence to test your FSM in the simulation and on the hardware board.

Pattern to be matched: **111111**

Input for testing: **01101111111001111110**